

Physical Sciences 3

Lectures 5 and 6 - February 20, 2008 - Voltage, Current, Resistance, Capacitance
Reading for Understanding: Chapter 24 and Chapter 26 s1-3

ELECTRIC CURRENT, I

the amount of charge, Q , going through a cross-section of a conductor

$$I = \frac{Q}{t}$$

measured in Amperes, A (in most metals, e^- are free to move around.)
units $\frac{C}{s} = A$

relationship

OHM'S LAW

current, I , flowing through a conductor is proportional to the potential difference ΔV between the ends.

$$\Delta V = RI \quad (\text{units: volts})$$

where R is a proportionality constant called RESISTANCE

$$[R] = \frac{V}{A} = \text{ohm}, \Omega$$

depends on the length, l , the cross sectional area, A as well as temperature and pressure of the material.

$$\therefore R = \rho \frac{l}{A} \quad (\text{units: ohms})$$

where ρ is called RESISTIVITY - a material constant, independent of shape.


EMF, Electromotive Force

not *really a force* but a device that converts one type of energy to another is a source of emf, like a battery \mathcal{E}

ability to create a potential diff

in practice

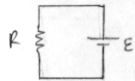put our chosen emf, a battery \mathcal{E} into a circuit connected to a resistor, R



current should be $E = IR$

* BUT batteries also have their own internal resistance, called "r" that decreases the available electrical energy

ELECTRIC POWER

recall that power is energy per unit time.

in a circuit, t seconds later, charge ($Q = It$) moves across ΔV losing energy $U = Q\Delta V$

$$P = \frac{U}{t} = \frac{Q\Delta V}{t} = I\Delta V$$

measured in watts

$$P = IV = I^2R = V^2/R$$

RESISTORS

① in series, current flow is the same through both resistors
 $I = I_1 = I_2$
voltages add across resistors:
 $E = V_1 + V_2$


finding the equivalent resistance:
 $R_1 + R_2 = R_{equiv}$

② in parallel, voltage across each resistor is the same
 $E = V_1 = V_2$
currents add across resistors:
 $I = I_1 + I_2$

finding the equivalent resistance:
 $1/R_1 + 1/R_2 = 1/R_{TOT}$

NEW TOPIC

CAPACITORS

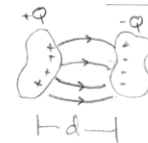

consists of two conducting objects separated by small distance, d .

purpose is to store electric charge, Q
also need an emf to create a potential difference - still a battery \mathcal{E}

$$Q = C\Delta V$$


where C is called CAPACITANCE measured in Farads (F) common unit is μF .

consider

PARALLEL-PLATE CAPACITOR

consider Gaussian surface around one plate... $\Phi_E = \frac{Q_{in}}{\epsilon_0} = \frac{Q}{\epsilon_0 A} = \vec{E} \cdot \vec{S}$
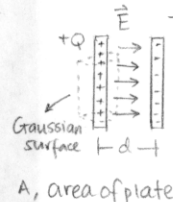
$$\vec{E} = \frac{Q}{\epsilon_0 A} \quad \Delta V = \frac{Qd}{\epsilon_0 A} \quad C = \frac{\epsilon_0 A}{d}$$



A, area of plate

IF put a dielectric material in between plates (width d) then...

$$\vec{E} = \frac{Q}{\kappa \epsilon_0 A} \quad \Delta V = \frac{Qd}{\kappa \epsilon_0 A} \quad C = \frac{\kappa \epsilon_0 A}{d}$$

CAPACITORS

① in series, charge is the same on both capacitors
 $Q = Q_1 = Q_2$
potentials add across capacitors:
 $E = V_1 + V_2$

finding the equivalent capacitance
 $1/C_{TOT} = 1/C_1 + 1/C_2$

② in parallel, potential across each capacitor is the same
 $V_1 = V_2 = E$
charge adds across capacitors
 $Q = Q_1 + Q_2$

finding equivalent capacitance:
 $C_{TOT} = C_1 + C_2$

ENERGY STORAGE

$$dW = dq \Delta V = dq \frac{Q}{C} \quad \text{integrate}$$

$$W = U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2$$

measured in joules