

Physical Sciences 3

Lectures 7 and 8 - February 27, 2008 - Kirchhoff's Rules and RC Circuits


Reading for Understanding: Chapter 26 s1-3, 5

DC CIRCUITS

- characterized by constant current, both in magnitude and direction.
- only resistors and emfs matter

add H

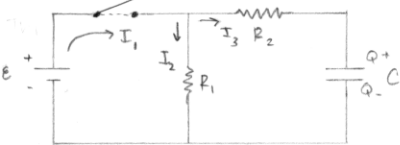what happens when you now put a capacitor in series with a resistor in a DC circuit?



call this an "RC CIRCUIT"

Consider the circuit above with an open switch first. (i.e. nothing flowing)

We know that capacitors store charge not current. \therefore a capacitor cannot conduct current. A capacitor also cannot store charge forever - it dissipates over time.

$$Q(t) = \int_0^t \frac{dQ}{dt} dt = Q_0 \quad \therefore I_c = 0$$

↑
definition of current I

initially, when the switch is first closed we are under CHARGING CONDITIONS

at $t=0$, C has charge Q_0 $\Delta V = \frac{Q}{C}$

$I = \frac{\Delta V}{R} = \frac{Q}{RC}$ \rightarrow time constant: time it takes for the (to 63%) capacitor to charge or discharge. The larger the R the larger it takes to charge. The larger the C the more storage there is.

so current is flowing through the resistor - it is dissipating through the resistor until $I_c = 0$, point at which the capacitor is fully charged.

$$I = -\frac{dQ}{dt} = \frac{Q}{RC} \rightarrow -\frac{1}{RC} dt = \frac{1}{Q} dQ \rightarrow \ln Q = -\frac{1}{RC} t + \text{constant}$$

$$Q(t) = Q_0(e^{-t/RC}) \quad \therefore I(t) = \frac{Q_0}{RC}(e^{-t/RC})$$

method \rightarrow KIRCHHOFF'S RULES

Specifically for solving emf/resistor circuits.

① IDENTIFY THE CURRENTS:

The emf \mathcal{E} is positive if current is flowing like so:



It doesn't matter which direction you ultimately choose; if you have the sign wrong, you know it'll be going in the opposite direction if it's negative.

② JUNCTION RULE: (NODES • A • B)

The sum of all the currents entering a junction equals the sum of all the currents leaving that junction.

look at • A $I_3 = I_1 + I_2$ • B $I_1 + I_2 = I_3$

③ LOOP RULE:

The sum of changes in potential around any closed path is zero

look at loop 1: (top half of circuit)


$$-R_1 I_1 + \mathcal{E}_1 - R_3 I_3 - R_2 I_2 = 0$$

look at loop 2: (bottom half of circuit)


$$\mathcal{E}_2 - R_5 I_2 - R_4 I_2 + \mathcal{E}_1 - R_3 I_3 - R_2 I_2 = 0$$

* YOU NOW HAVE 3 EQUATIONS \rightarrow 3 UNKNOWNNS! SOLVE! *

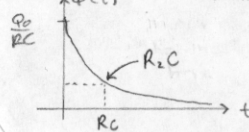
so the resistor's current (I_3) falls off: (part that in series with H)



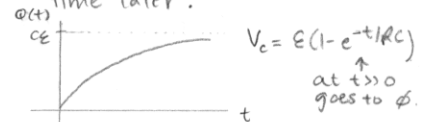
AS I_3 dissipates, the capacitor is charging up, until $\Delta V = \mathcal{E}$ some time later:



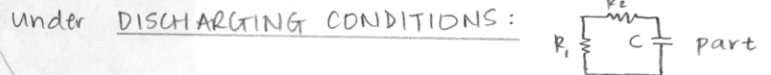Now, after the capacitor has been fully charged, let's open the switch momentarily... then let's close it; we are under DISCHARGING CONDITIONS:



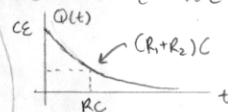now all the charge in the capacitor discharges (dissipates) via both the resistors in the circuit ($V_c = V_0 e^{-t/RC}$ and $Q = Q_0 e^{-t/RC}$)



SO Kirchhoff for left and right loops? $I_1 = I_2 + I_3$

LHS: $\mathcal{E} - R_1 I_2 = 0$ RHS: $I_3 = \frac{dQ}{dt}$ so $R_1 I_2 - R_2 I_3 + \frac{Q}{C} = 0$

$$\mathcal{E} - R_2 \frac{dQ}{dt} + \frac{Q}{C} = 0$$

solve differential ...