

Physical Sciences 3


Lectures 9 and 10 - March 5, 2008 - Fourier Series and RC Filters

FOURIER SERIES

Theorem: any periodic function and therefore any function over a finite range can be expressed as a series of sines and cosines.

$$f(x) = f(x + 2\pi)$$
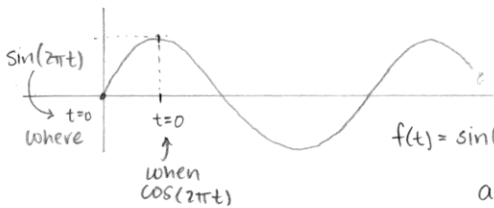
$$f(x) = \frac{a_0}{2} + \sum_{n=1}^{\infty} a_n \cos(nx) + b_n \sin(nx)$$



$$f(t) = \sin(t + \phi)$$

↑ arbitrary phase shift

$$\phi = \frac{\pi}{2} \text{ makes } \cos(t)$$

$$\sin(t + \phi) = \sin t \cos \phi + \cos t \sin \phi$$


Now in terms of angular frequency, $\omega = 2\pi f$

$\sin(2\pi f t)$ or $\cos(2\pi f t)$ in radians

$\sin(\omega t)$ or $\cos(\omega t)$


EXAMPLE FUNCTIONS

• sawtooth function

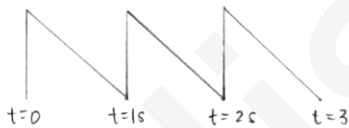

$$f(t) = \sin(2\pi t) + \frac{\sin(2 \times 2\pi t)}{2} + \frac{\sin(3 \times 2\pi t)}{3} + \dots$$


• squarewave function

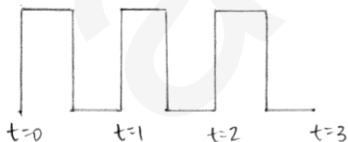

$$f(t) = \sin(2\pi t) + \frac{\sin(3 \times 2\pi t)}{3} + \frac{\sin(5 \times 2\pi t)}{5}$$

THE CONNECTION TO:

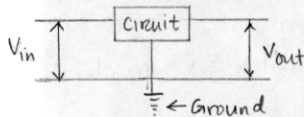It is useful to make electrical circuits that respond differently to different frequencies. Electrical circuits transform an input wave form into an output wave form



* this ΔV or $V_{in} - V_{out}$ is time-varying voltage \odot gives AC - alternating current - circuit.

* When a circuit has a resistor and capacitor to ground, called an RC filter.

RC FILTERS

* Isolation of frequencies *



Two types of filters: HIGH & LOW PASS

the output amplitude is roughly half that of the input is the frequency $\frac{1}{2\pi RC}$



→ where $\omega = \frac{1}{RC}$ cut-off

possible: amplitude Δ phase Δ

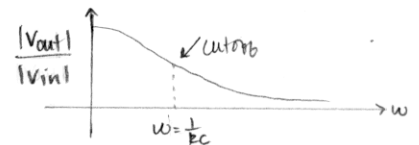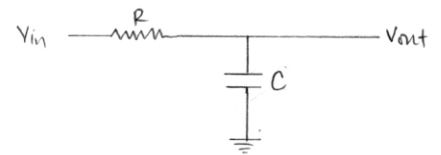LOW PASS: frequencies below the cutoff frequency pass, those higher are attenuated.



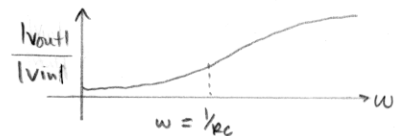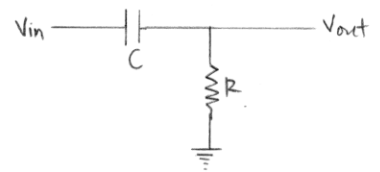HIGH PASS: frequencies above the cutoff frequency pass, those lower are attenuated.



$$V_{in}(t) = V_0 \sin \omega t = IR + \frac{Q}{C}$$

$$V_{out}(t) = \frac{Q}{C} = A \sin \omega t + B \cos \omega t$$

$$V_{in}(t) = RC + \frac{dV_{out}(t)}{dt} + V_{out}(t)$$

$$\therefore V_0 \sin \omega t = (A - RC\omega) \sin \omega t + (B + RC\omega) \cos \omega t$$